

Experiment 2: Half adder and Full adder Implementation in VHDL.

Digital Systems Design Lab



INDIAN INSTITUTE OF INFORMATION TECHNOLOGY SONEPAT

भारतीय सूचना प्रौद्योगिकी संस्थान, सोनीपत

(An Institute of National Importance under an Act of Parliament)

Submitted To:
Dr. Rajiv Verma
Assistant Professor
IIIT Sonapat

Submitted By:
Gaurav Yadav
CSE
11911038

❖VHDL Source Code for Half Adder and Full Adder:

--BY Gaurav Yadav | 11911038 | CSE

Library ieee;

use ieee.std_logic_1164.all;

entity half_adder is

port(a1,b1:in bit;

sum1,carry1:out bit);

end half_adder;

entity full_adder is

port(a2,b2,c2:in bit;

sum2,carry2:out bit);

end full_adder;

architecture data of full_adder is

begin

sum2<= a2 xor b2 xor c2;

carry2 <= ((a2 and b2) or (b2 and c2) or (a2 and c2));

end data;

architecture data of half_adder is


begin

sum1<= a1 xor b1;


carry1 <= a1 and b1;

end data;

❖Output Waveform of Half Adder:

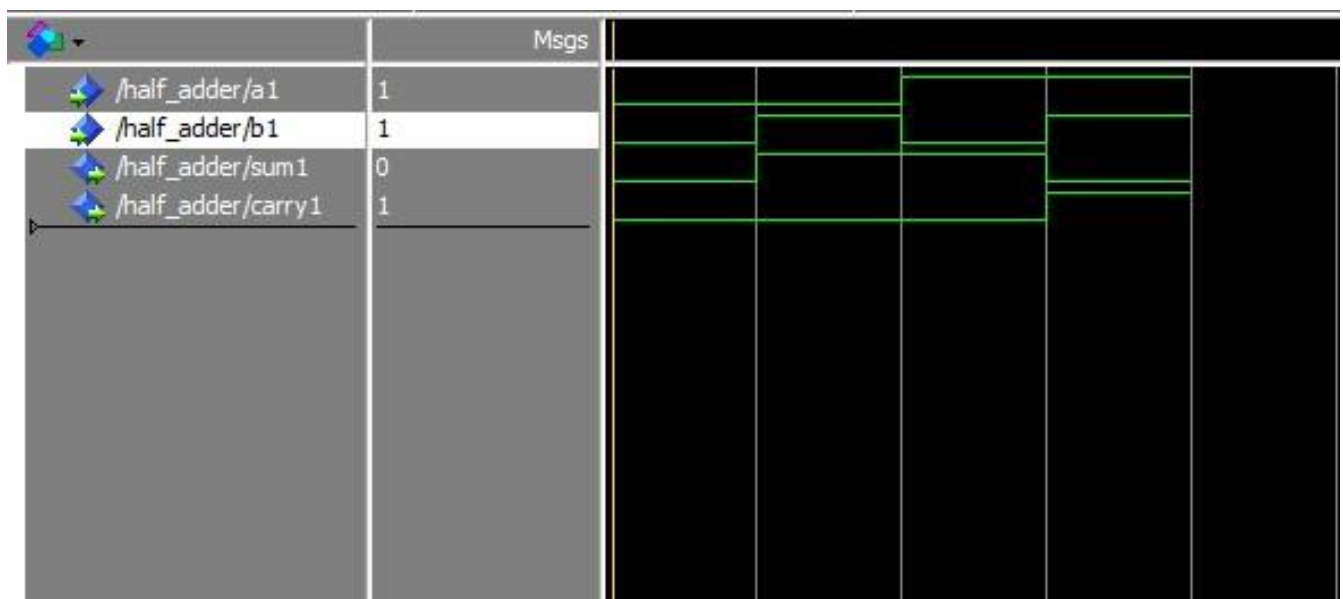

❖ **Output Waveform of Full Adder:**

 

❖ **Result:**

With the help of this experiment, we are able to understand the behaviour of half adder and full adder digitally.